

Computer Organization and Architecture Laboratory

Assignment-3


Group members (Group - 56):

- 1. Utsav Mehta (20CS10069)**
- 2. Vibhu (20CS10072)**

Design of an Ripple Carry Adder (RCA) :-

A. Half - adder:

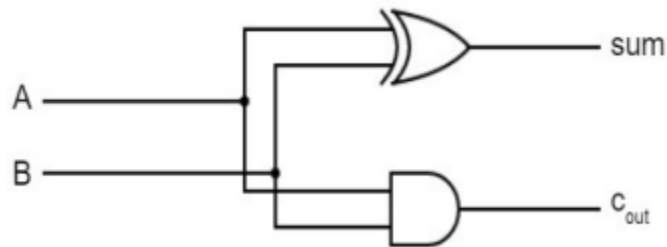
- a. Takes two input bits 'a' and 'b'
- b. Produces two output bits 'sum' and 'carry'
- c. Values of the output bits can be derived from the input bits as -
 - i. $\text{sum (or s)} = a \oplus b$ (bitwise - xor operation)
 - ii. $\text{carry (or c)} = a \& b$ (bitwise - and operation)
- d. The logic circuit for half adder is:



- e. The truth table for half - adder is as shown -

| Truth Table (for half adder) | | | |
|------------------------------|---|--------|-------|
| Input | | Output | |
| A | B | Sum | Carry |
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |


- e. The graph observed is as shown -

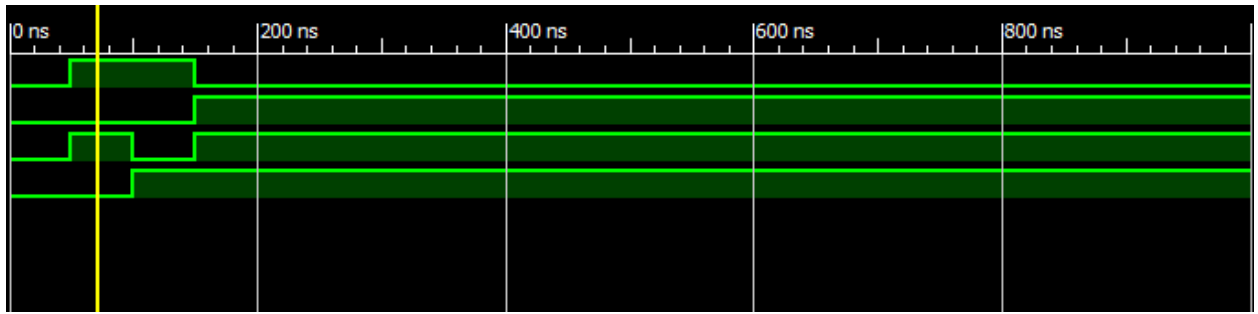

Relevant files: half_adder.v, tb_half_adder.v

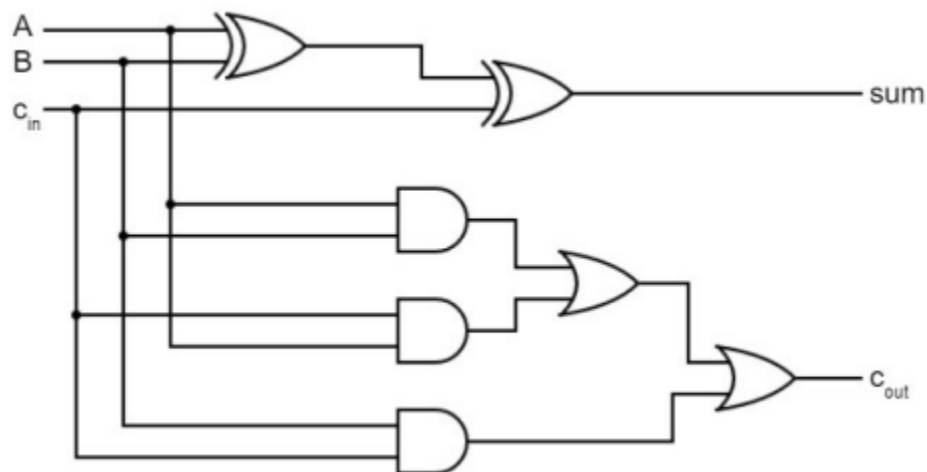B. Full - adder:


- Takes three input bits 'a', 'b' and 'carry0'
- Produces two output bits 'sum' and 'carry1'
- Values of the output bits can be derived from the input bits as -
 - $\text{temp_sum} = a \oplus b$
 - $\text{temp_carry0} = a \& b$
 - $\text{sum} = \text{temp_sum} \oplus \text{carry0}$
 - $\text{temp_carry1} = \text{temp_sum} \& \text{carry0}$
 - $\text{carry1} = \text{temp_carry0} \vee \text{temp_carry1}$
- The logic circuit for full adder is as shown:



- The truth table for full - adder is as shown -

| Truth Table (for Full Adder) | | | | |
|------------------------------|---|--------|---------|--------|
| Inputs | | | Outputs | |
| A | B | Carry0 | Sum | Carry1 |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |


f. The graph observed is as shown -

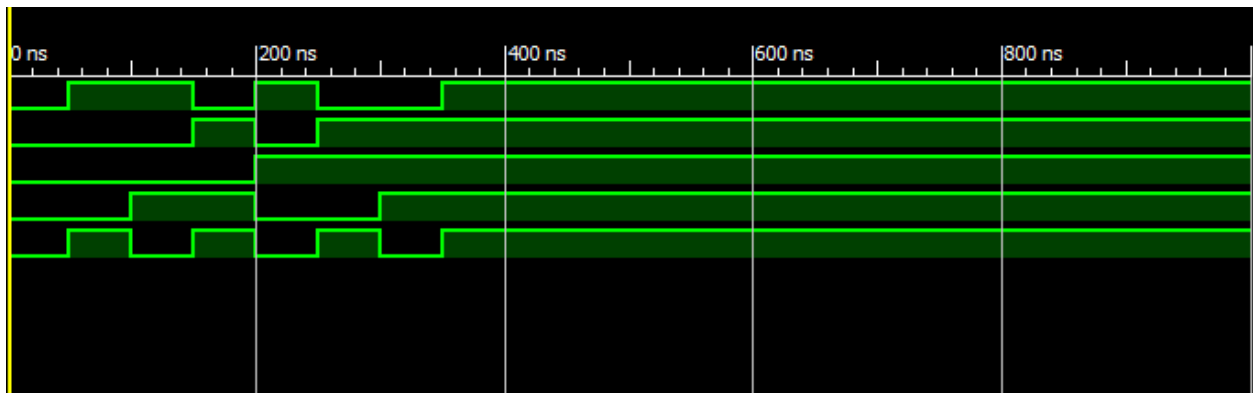


Relevant Files: full_adder.v, tb_full_adder.v

C. Ripple Carry Adders:

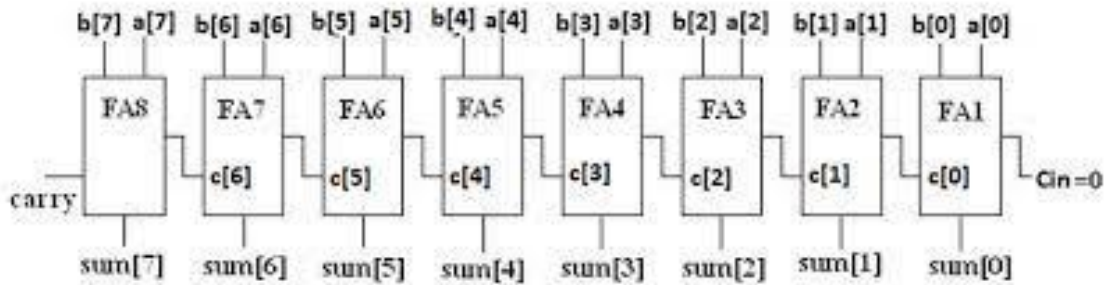
- a. 8-bit adder - Take 8 full adders and connect them in cascading fashion



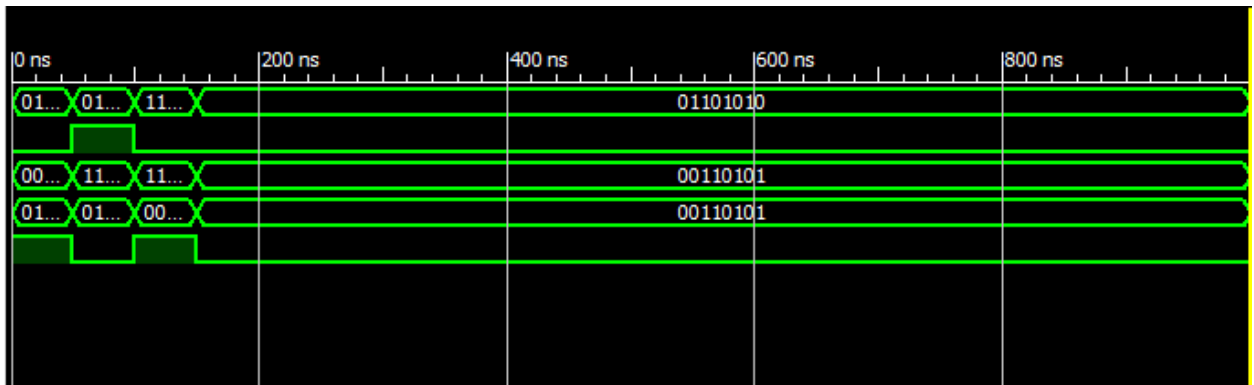
The graph observed for 8-bit ripple carry adder is as shown -



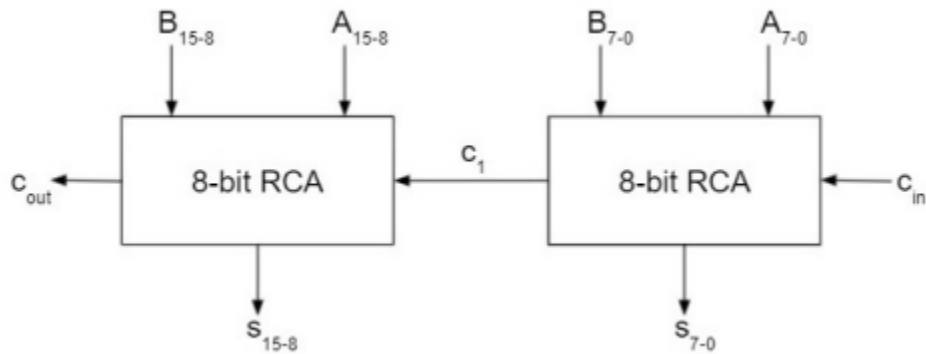
- b. 16-bit adder - Take 2 eight bit adders and connect them in cascading fashion



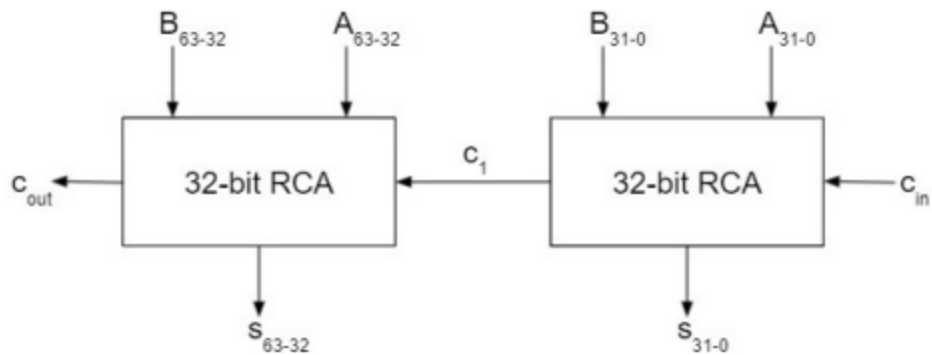The graph observed for 16-bit ripple carry adder is as shown -



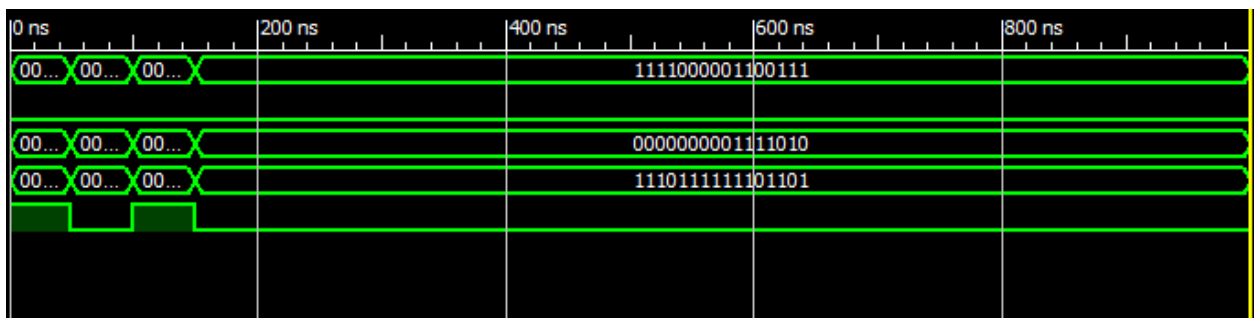The graph observed for 64-bit ripple carry adder is as shown -



The synthesis report (denoting the longest delays in the circuits is):-

| Synthesis report | |
|--------------------|---------------|
| Ripple carry adder | Longest delay |
| Half bit adder | 1.066 |
| Full bit adder | 1.246 |
| 8-bit RCA | 3.471 |
| 16-bit RCA | 6.167 |
| 32-bit RCA | 11.559 |
| 64-bit RCA | 22.343 |

Relevant Files:

s8_bit_adder.v, tb_8_bit_adder.v

s64_bit_adder.v, tb_64_bit_adder.v

D. Using the above circuit for calculating differences:

Let the input integers be A and B, and we want to calculate the value of A-B using the ripple carry adders generated above.

The equation can be re-interpreted as $A + (-B)$.

The value of $-B$ can be computed from B by the following steps:

1. Take the two's complement of B
2. Add 1 to the value computed above

Thus, we can add the generated value and A to compute the difference between A and B.

The graph observed for 64-bit ripple carry adder (used as a subtractor) is as shown -

| | | |
|------------|----------------------------------|----------------------------|
| XX...00... | 00000000000000000000000000000000 | 00001000110110010010001100 |
| XX...00... | 00000000000000000000000000000000 | 00001000110110010111100000 |
| XX...11... | 11111111111111111111111111111111 | 111111111111111010101011 |

Relevant Files:

subtractor.v, s64_bit_adder.v

Design of an Carry-Look Ahead (CLA) adder :-

A. Design of a 4-bit CLA –

- a. A Carry-Look Ahead adder improves the time taken by a Ripple Carry Adder by computing the carry for each subsequent step beforehand.
- b. The hardware for CLA is more complex than that of RCA.
- c. We introduce two variables, for pre-computation of the carry - Propagate (P) and Generate(G)

$$G_i = A_i \cdot B_i \text{ (carry generate)}$$

$$P_i = A_i \oplus B_i \text{ (carry propagate)}$$


- i. G_i denotes the carry generation at the i th stage, computed independently from other bits.
- ii. P_i denotes the propagation of carry from this stage, to the next, thus we can write the following -

$$C_{i+1} = G_i + P_i \cdot C_i$$

- d. The Boolean equations for Look Ahead carry generation are -

 - i. $c[0] = c_in$
- ii. $c[1] = g[0] \mid (p[0] \& c_in)$
- iii. $c[2] = g[1] \mid (p[1] \& g[0]) \mid (p[1] \& p[0] \& c_in)$
- iv. $c[3] = g[2] \mid (p[2] \& g[1]) \mid (p[2] \& p[1] \& g[0]) \mid (p[2] \& p[1] \& p[0] \& c_in)$
- v. $c[4] = g[3] \mid (p[3] \& g[2]) \mid (p[3] \& p[2] \& g[1]) \mid (p[3] \& p[2] \& p[1] \& g[0]) \mid (p[3] \& p[2] \& p[1] \& p[0] \& c_in)$
- vi. $c[4] = c_out = \text{carry out bit}$

Circuit Diagram for a 4-bit CLA is as shown -



Relevant files:- CLA_4_bit.v, tb_CLA_4_bit.v

B. Comparison of a 4-bit CLA with 4-bit RCA –

The speed (or time) required by a 4-bit CLA vs 4-bit RCA, for the same input bits, is as shown -

| Synthesis Report | |
|------------------|-----------------|
| 4-bit CLA | 4-bit RCA |
| 2.123ns | 2.115ns |
| 0.249ns (logic) | 0.249ns (logic) |
| 1.874ns (route) | 1.866ns (route) |


The time required by a RCA is clearly greater than that required by a CLA, as the delay for shifting carry from (i)th bit to (i+1)th is minimized. Thus CLAs provide a faster method to implement bitwise summations, by decreasing the rippling costs.

Relevant files:- CLA_4_bit.v, tb_CLA_4_bit.v
s4_bit_adder.v (4-bit RCA)
tb_4_bit_adder.v (test bench for 4bit RCA)
full_adder.v, half_adder.v

C. Design of a 16-bit CLA and it's comparison with 16-bit RCA –

a. Augmenting the 4-bit CLA to generate Propagate and Generate Signals -

 - i. Propagate (P) - block propagate for the next level of hierarchy
- ii. Generate (G) - block generate for the next level of hierarchy
- iii. The augmented 4-bit circuit looks like -




Relevant Files(s): CLA_4_bit.v, s4_bit_adder.v (4bit RCA)

b. Designing a 16-bit CLA using Look Ahead Carry Unit

i. Look Ahead Carry Unit -

1. Input - block propagates and generates from the previous level
2. Output - carry bits and block propagate, generate for the next level

 ii. 4-bit CLA augmented circuit is integrated with Look Ahead Carry unit to create a 16-bit Carry Look Ahead adder



Relevant File(s): carry_look_ahead.v,
tb_carry_look_ahead.v, CLA_16_bit.v,
tb_CLA_4_bit.v

c. Comparison of the circuit created by 16-bit Carry Look Ahead adder (using carry look ahead unit, and four 4-bit Carry Look augmented adders) and 16-bit Ripple Carry Adders (using four 4-bit CLA adders)


- i. Time required by the 16-bit CLA is utilized in computation the sum of four 4-bits by the 4-bit CLA augmented and the time required by the Carry Look

Ahead unit to transfer the carry between various 4-bit units.

- ii. Time required by the 16-bit RCA is utilized in the computation of the sum required by four 4-bit CLA and the time required by the Ripple Carry Units to transfer the carry from one unit to the other.
- iii. The time required to ripple the carry bits from one CLA to the other is the critical factor that results in the given time gaps –

| Synthesis Report (for 16-bit RCA) | |
|-----------------------------------|--------------------------|
| Using Carry Look Ahead unit | Using Ripple Carry Adder |
| 5.513ns | 6.167ns |
| 0.869ns (logic) | 0.993ns (logic) |
| 4.644ns (route) | 5.174ns (route) |

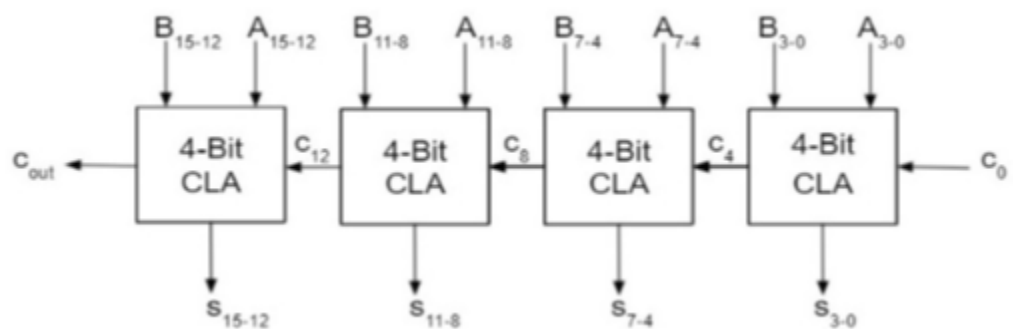The circuit for 16-bit CLA using ripple carry adder unit:



Relevant File(s): CLA_16_bit.v, tb_CLA_16_bit.v,
CLA_16_bit_ripple.v, tb_CLA_16_bit_ripple.v,
carry_look_ahead.v, tb_carry_look_ahead.v

- d. Result of Synthesis and the corresponding speed and LUTs
- i. Time required by the 16-bit CLA is utilized in computation the sum of four 4-bits by the 4-bit CLA augmented and the time required by the Carry Look Ahead unit to transfer the carry between various 4-bit units.
 - ii. Time required by the 16-bit RCA is utilized in the computation of the sum required by four 4-bit CLA and the time required by the Ripple Carry Units to transfer the carry from one unit to the other.
 - iii. Comparison of the cost required by the LUTs -
 1. Slice LUTs used for 16-bit CLA - 45 (without wrapper) and 52 (with wrapper)
 2. Slice LUTs used for 16-bit RCA - 24
 - iv. The time required and Look Up Tables (LUTs) by various adders including the RCAs generated in Part-1, and various adders generated for Part-2 are summarized below.

| Module | Total delay (in ns) | Logic Delay (in ns) | Route Delay (in ns) | LUTs used |
|-----------------------|------------------------|------------------------|------------------------|--------------|
| s4_bit_adder.v (RCA) | 2.115 | 0.249 | 1.866 | 5 |
| s8_bit_adder.v (RCA) | 3.471 | 0.497 | 2.974 | 12 |
| s16_bit_adder.v (RCA) | 6.167 | 0.993 | 5.174 | 24 |
| s32_bit_adder.v (RCA) | 11.559 | 1.985 | 9.574 | 48 |
| s64_bit_adder.v (RCA) | 22.343 | 3.969 | 18.374 | 96 |
| CLA_4_bit.v | 2.123 | 0.249 | 1.874 | 6 |

| | | | | |
|-------------------------------|-------|-------|-------|----|
| wrapper_CLA_4_bit.v | 2.116 | 0.756 | 1.360 | 6 |
| CLA_4_bit_augmented.v | 3.209 | 0.373 | 2.836 | 10 |
| wrapper_CLA_4_bit_augmented.v | 2.130 | 0.756 | 1.374 | 10 |
| CLA_16_bit.v | 5.513 | 0.869 | 4.644 | 45 |
| wrapper_CLA_16_bit.v | 3.411 | 1.004 | 2.407 | 52 |
| CLA_16_bit_ripple.v | 6.167 | 0.993 | 5.174 | 24 |
| wrapper_CLA_16_bit_ripple.v | 3.344 | 0.880 | 2.464 | 47 |